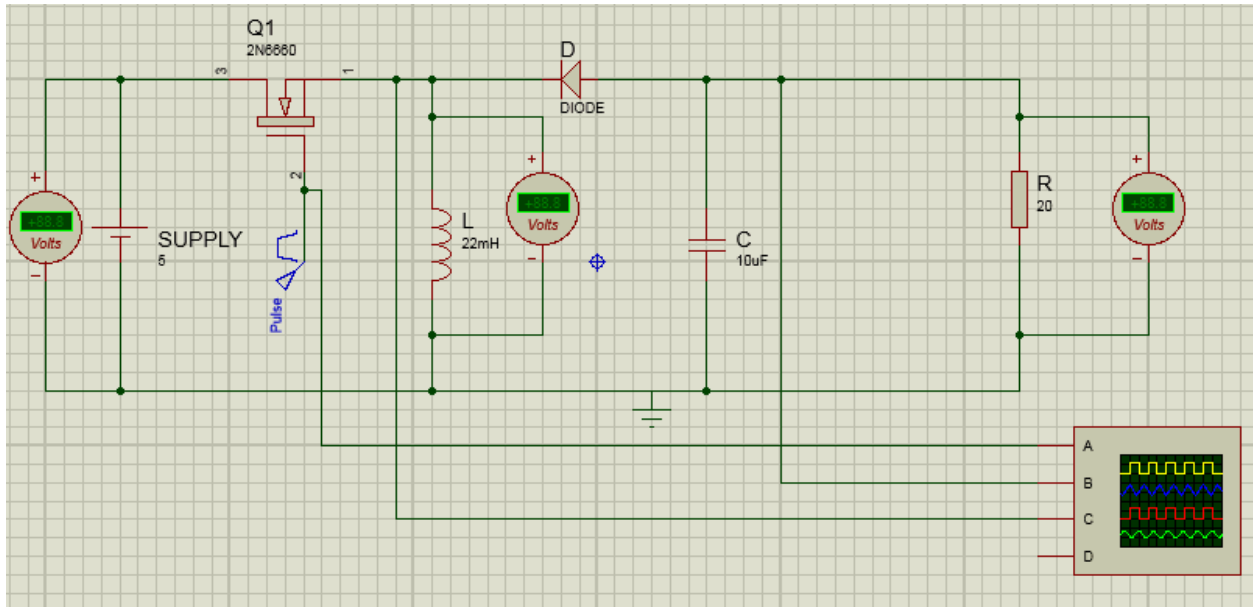


## Buck-Boost Converter Data

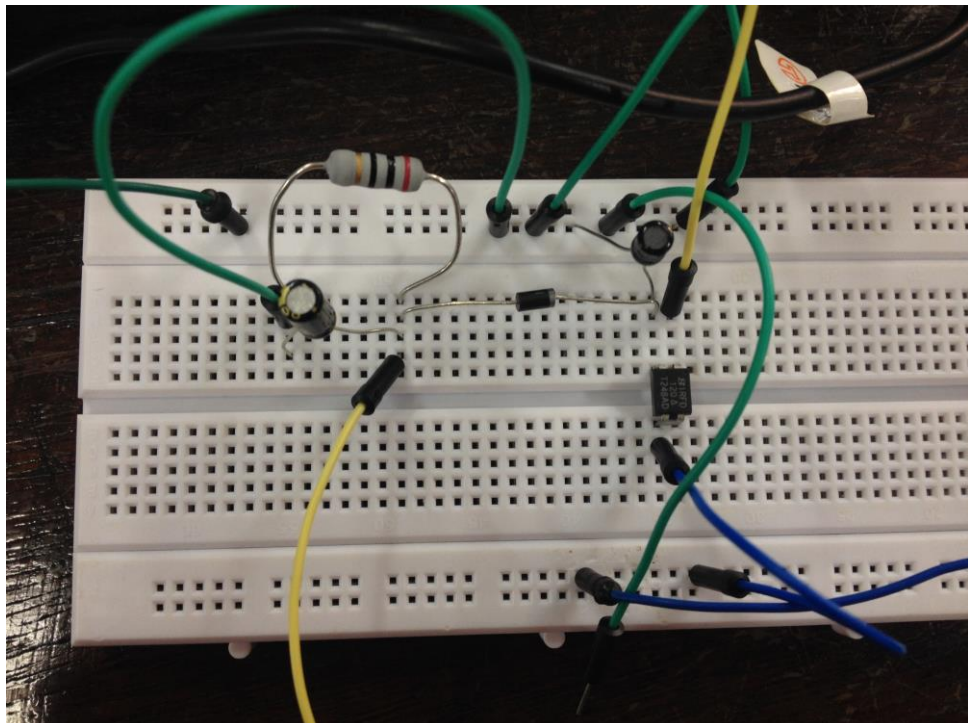



**Figure 1: Proposed Buck-Boost converter circuit**

The oscillator is connected to Pulse Generator (yellow), the voltages across inductor,  $V_L$  (red) and capacitor,  $V_C$  (blue).

$V_D$ : 5V

$V_G$ : 8V

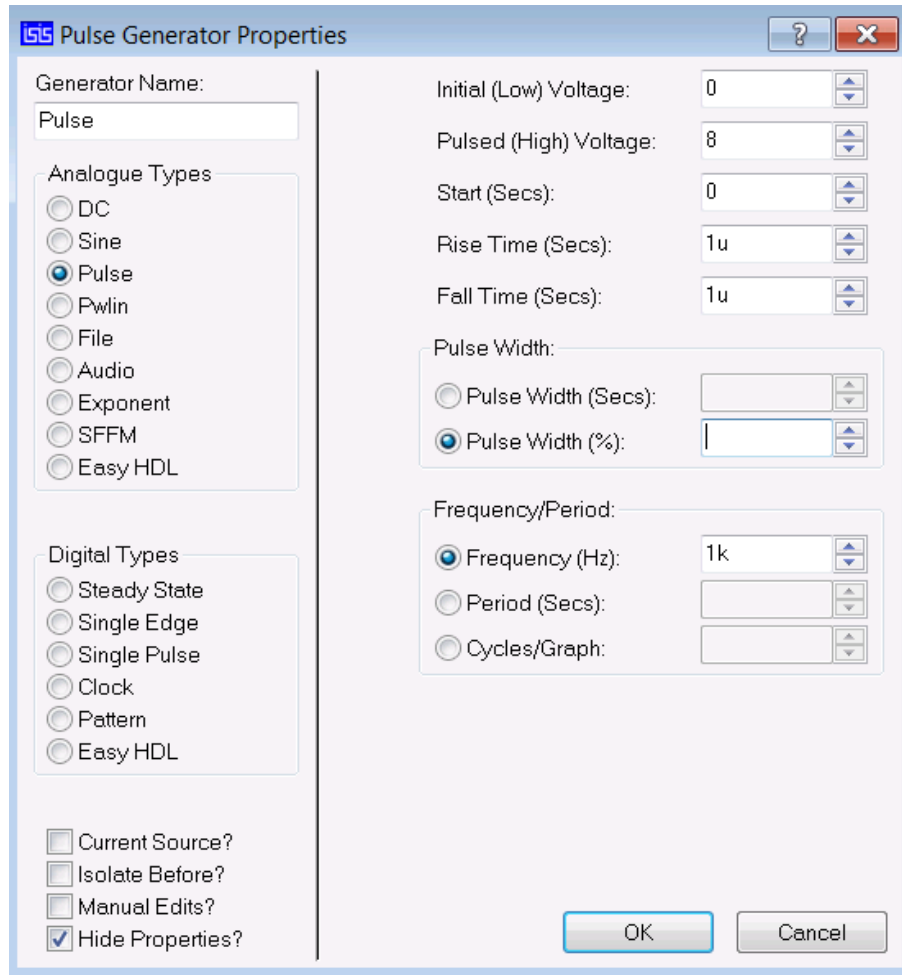

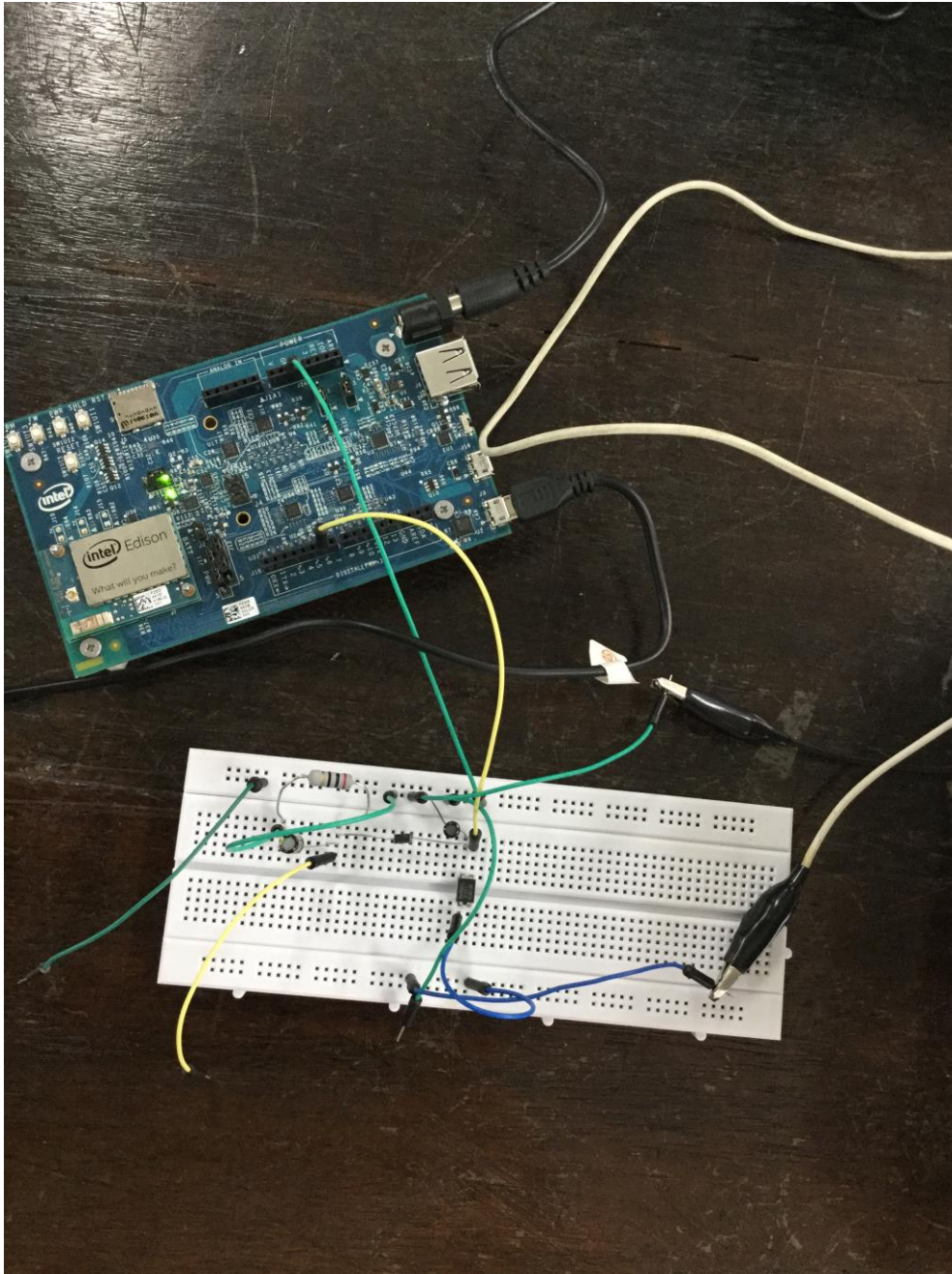


**Figure 2: Values are set for of  $t_{rise}$ ,  $t_{fall}$  and Frequency**

Duty Cycle	$V_L$
30%	(Buck)
50%	8V
80%	(Boost)

**Table 1: Output  $V_L$  for 30% of duty cycle at the gate**

## Circuit setup with Intel Edison



# Activity 1: set 30% duty cycle Edison PWM

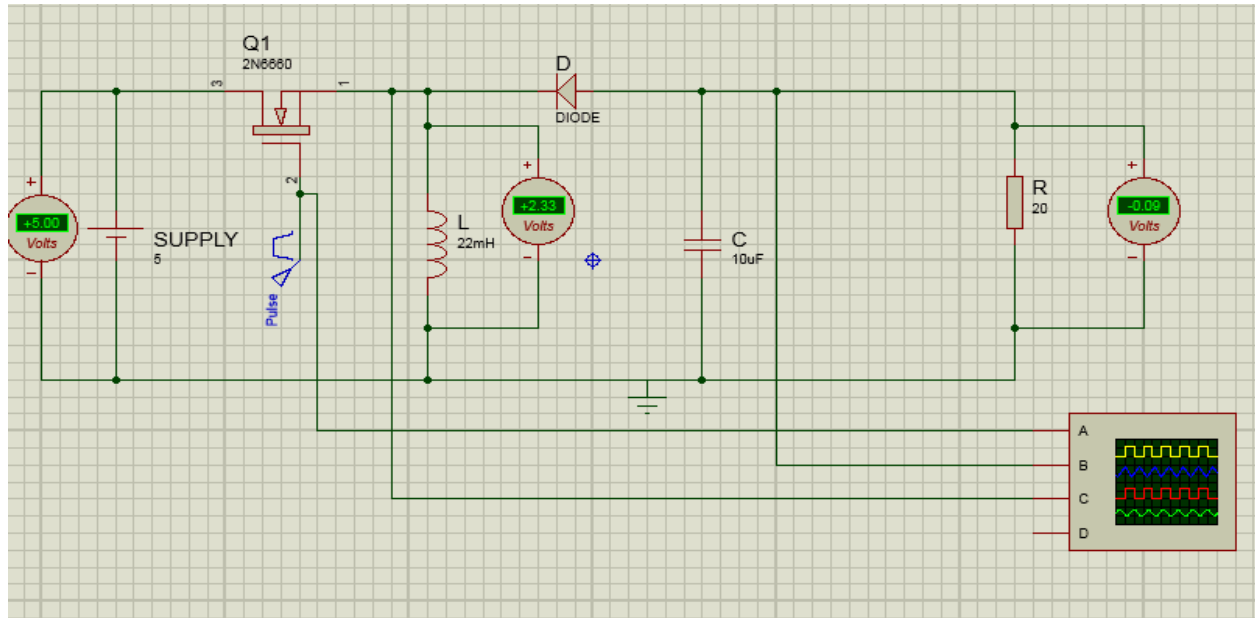


Figure 3: Output voltage across the inductor,  $V_L$  for 30% duty cycle


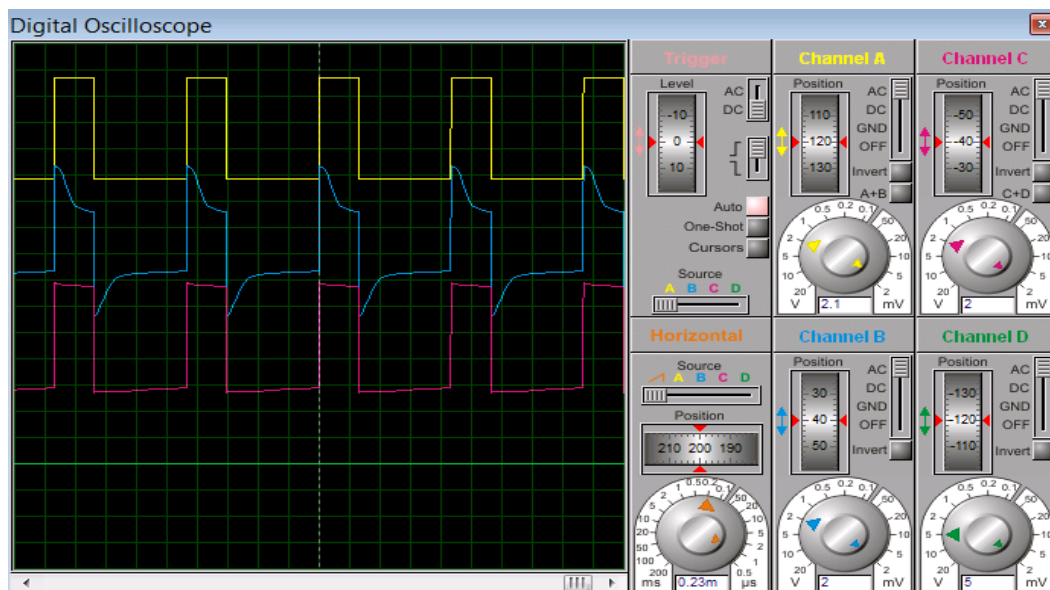


Figure 4: Example Output waveform for 30% duty cycle

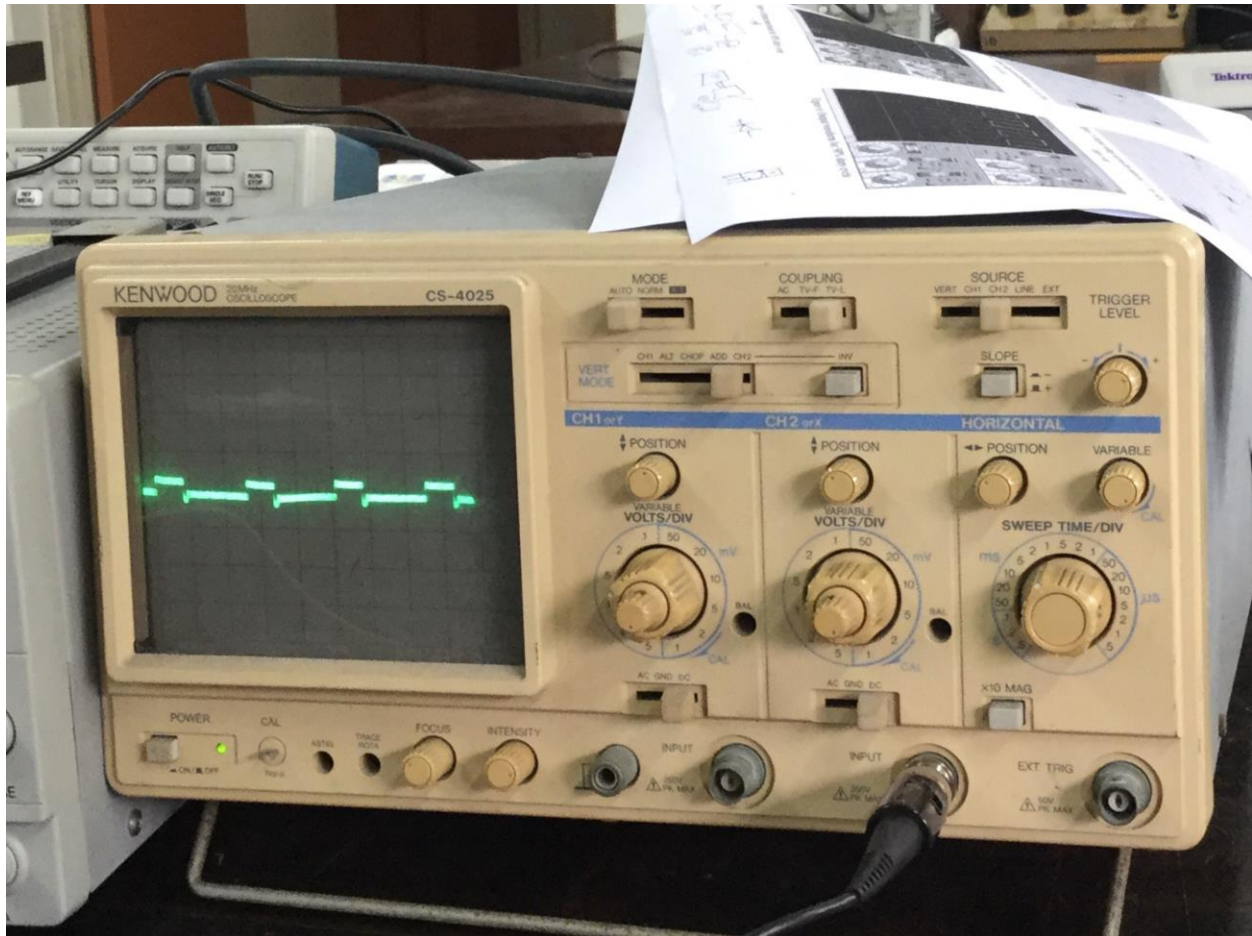

## Expectation observation: Input, 30% duty cycle



## Code testing

```
30.js x 50.js x 80.js x
1 var m = require('mraa');
2 console.log("Libmraa version: " + m.getVersion());
3
4 var generate = new m.Pwm(6); // hook up at PWM pin 6 at Edison
5 var dc = 0.3; // set duty cycle: 30%
6
7 generate.period_us(200); // set period as 200 ms
8 generate.enable(true);
9
10 setInterval(function() {
11     generate.write(dc);
12     console.log("duty cycle (%): " + dc * 100);
13 }, 1000);
```

## Activity 2: set 50% duty cycle Edison PWM

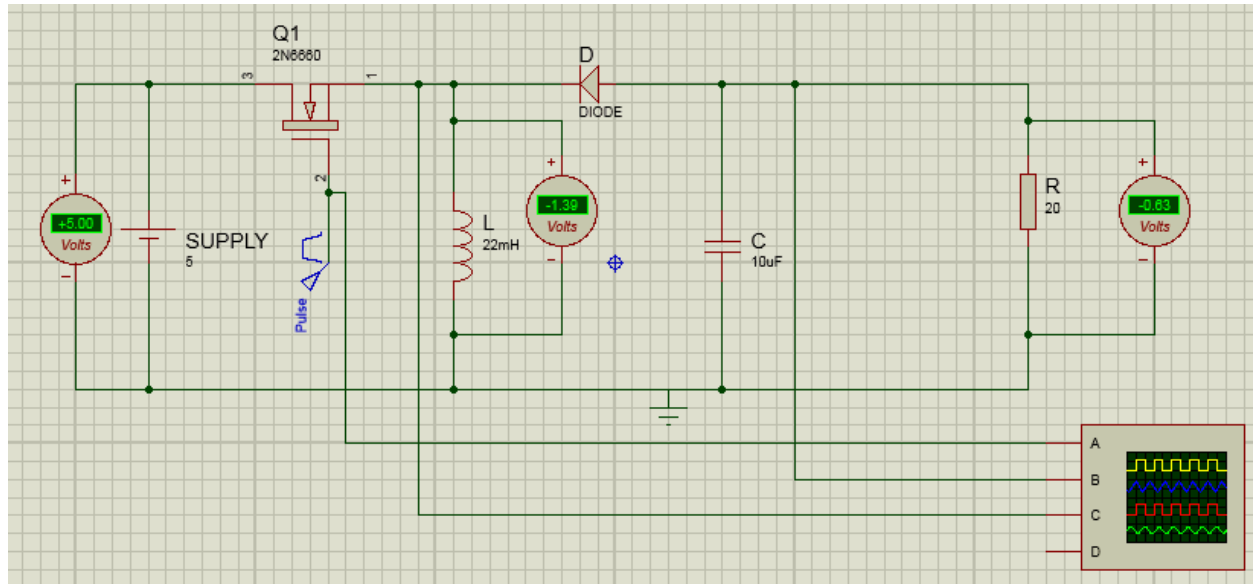


Figure 5: Output voltage across the inductor,  $V_L$  for 50% duty cycle


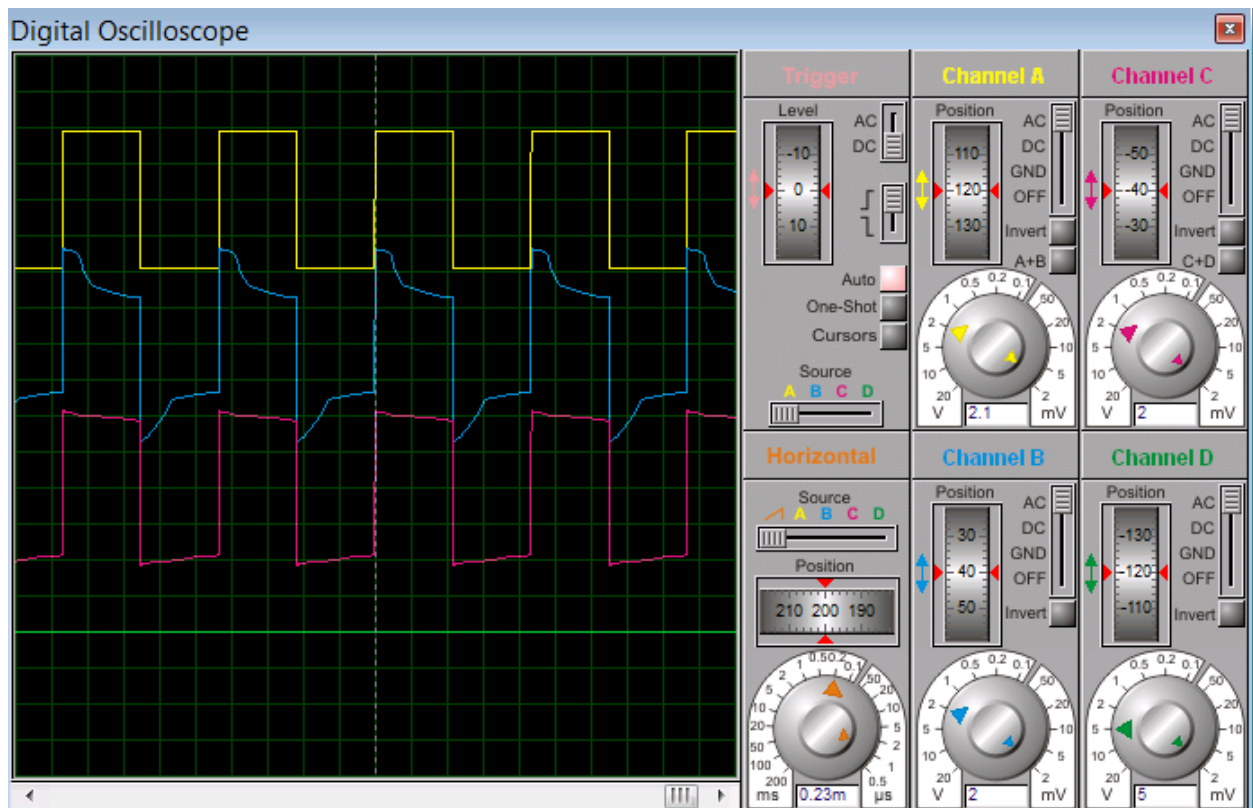


Figure 6: Example Output waveform for 50% duty cycle

## Expectation observation

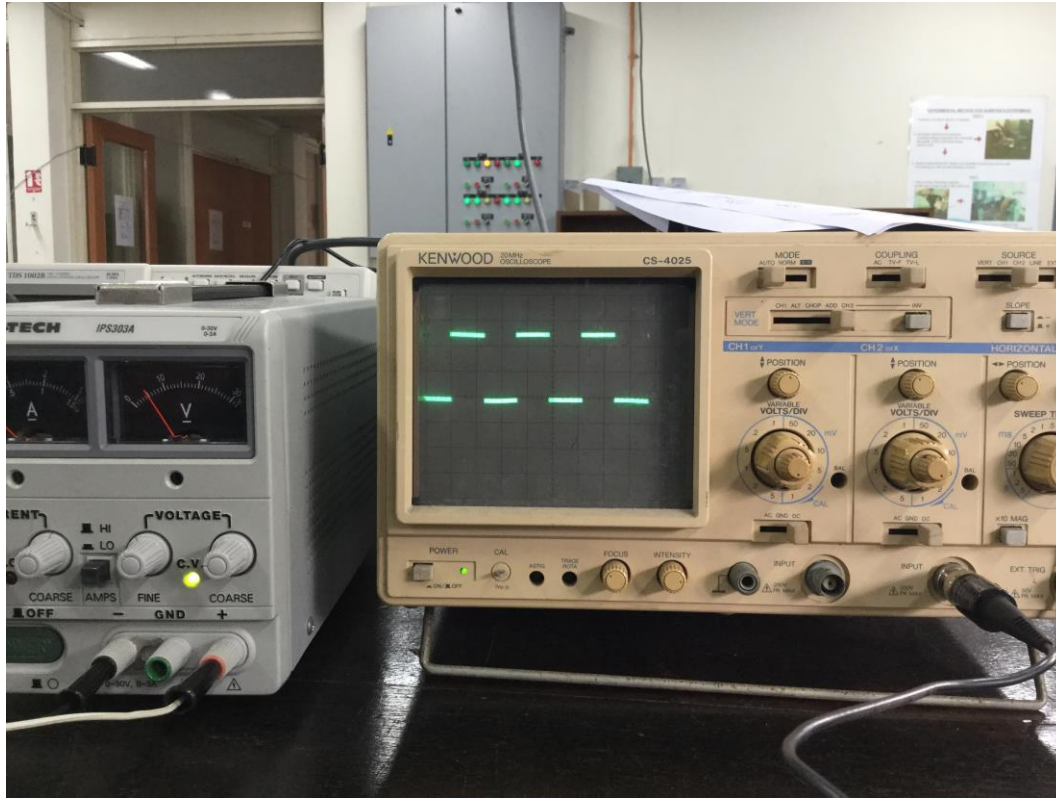

## Code testing

```
30.js 50.js 80.js
1 var m = require('mraa');
2 console.log("Libmraa version: " + m.getVersion());
3
4 var generate = new m.Pwm(6); // hook up at PWM pin 6 at Edison
5 var dc = 0.5; // set duty cycle: 50%
6
7 generate.period_us(200); // set period as 200 ms
8 generate.enable(true);
9
10 setInterval(function() {
11     generate.write(dc);
12     console.log("duty cycle (%): " + dc * 100);
13 }, 1000);
```

## Activity 3: set 80% duty cycle Edison PWM

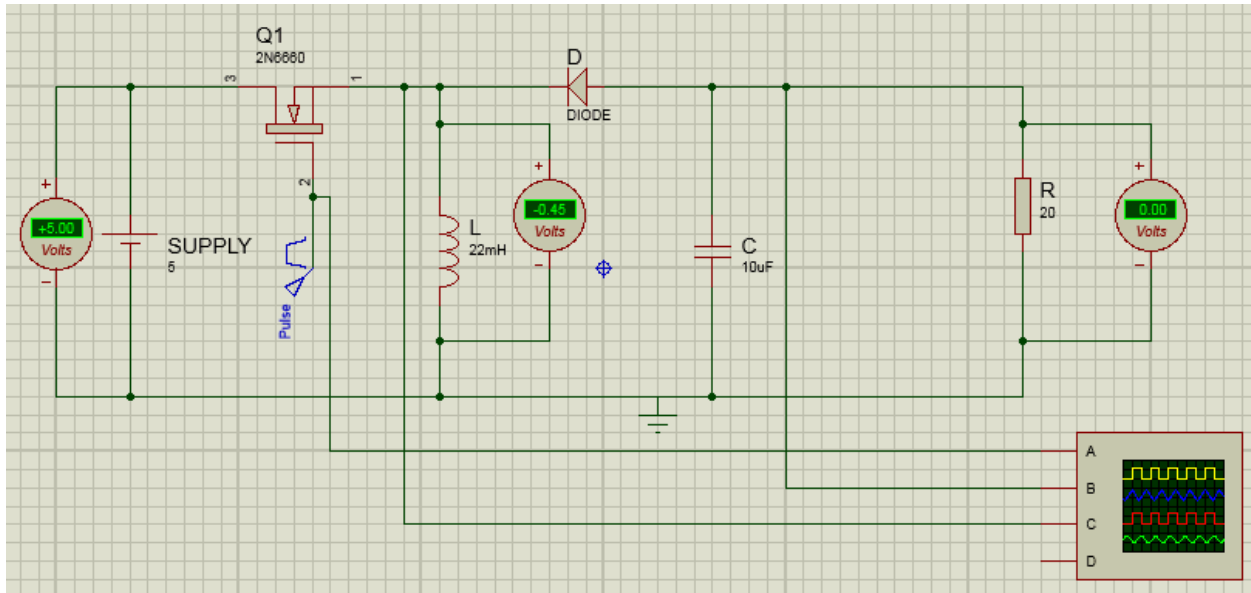


Figure 7: Output voltage across the inductor,  $V_L$  for 80% duty cycle


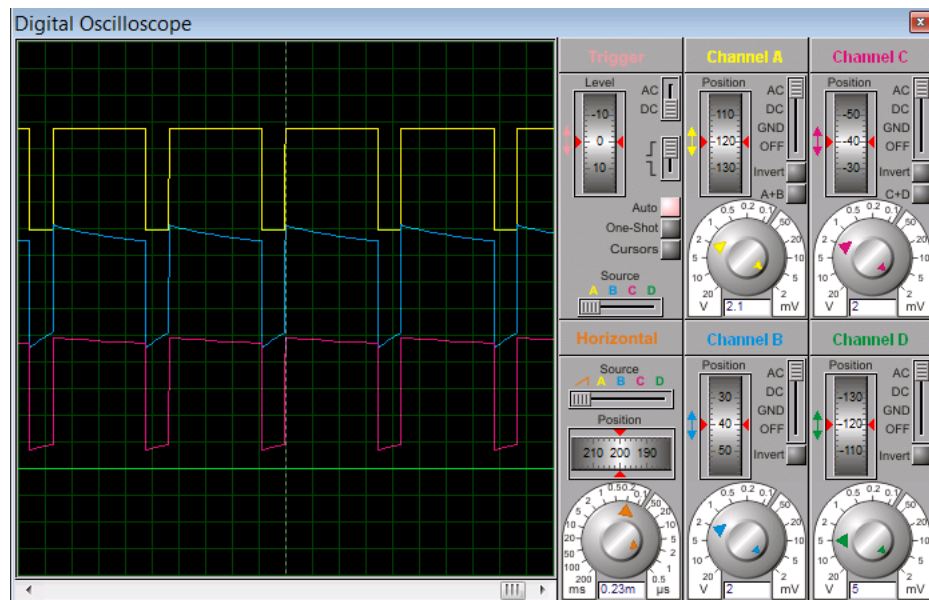



Figure 8: Sample Output waveform for 80% duty cycle

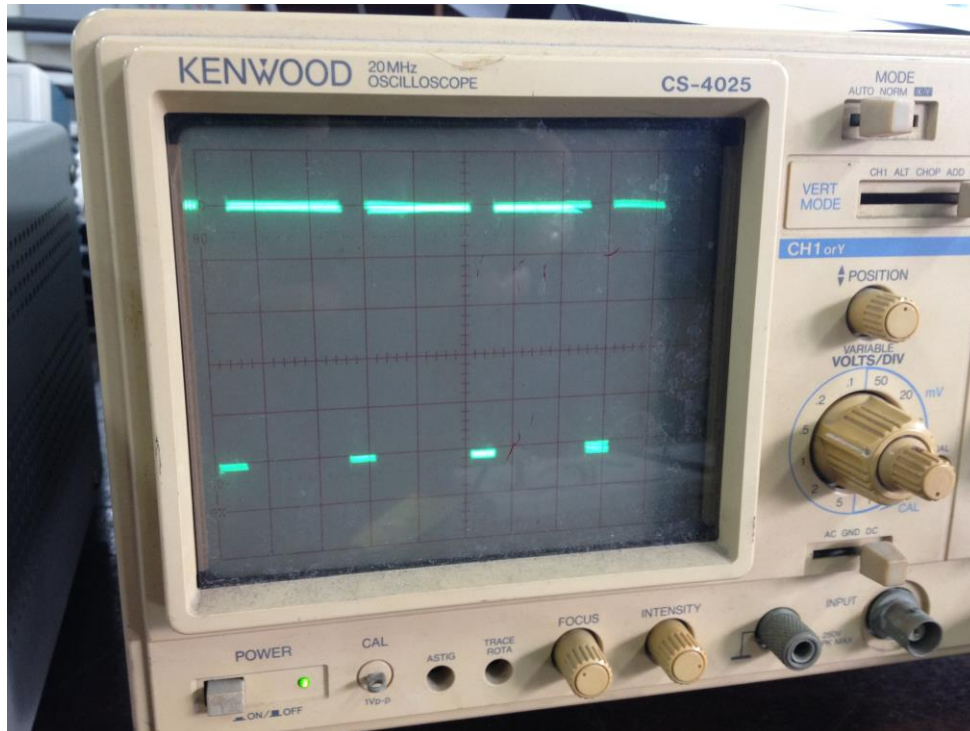


**Expectation: Input, 80% duty cycle**



**Expectation: Output, 80% duty cycle**

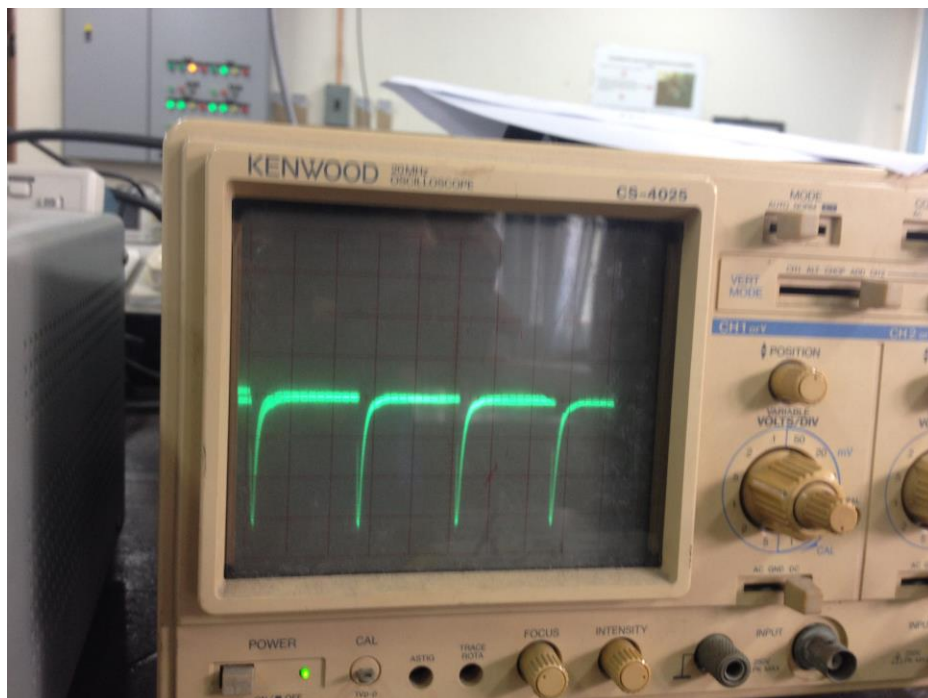

## Code testing

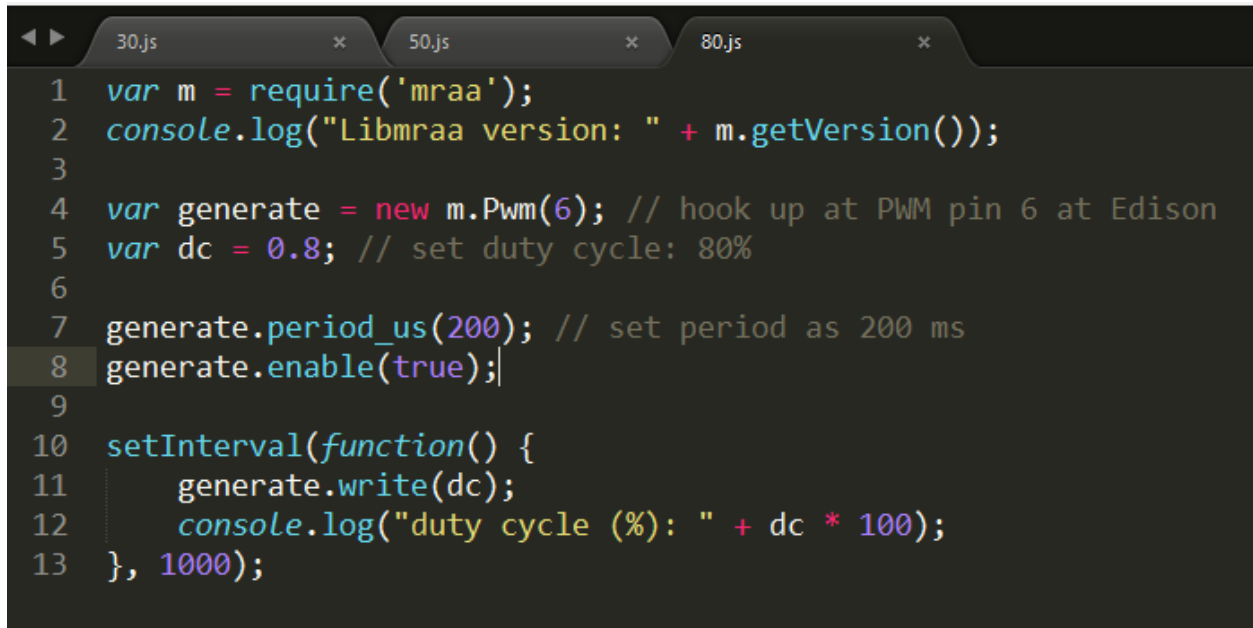

The image shows a code editor with three tabs: 30.js, 50.js, and 80.js. The 50.js tab is active. The code is as follows:

```
1 var m = require('mraa');
2 console.log("Libmraa version: " + m.getVersion());
3
4 var generate = new m.Pwm(6); // hook up at PWM pin 6 at Edison
5 var dc = 0.8; // set duty cycle: 80%
6
7 generate.period_us(200); // set period as 200 ms
8 generate.enable(true);
9
10 setInterval(function() {
11     generate.write(dc);
12     console.log("duty cycle (%): " + dc * 100);
13 }, 1000);
```

Prepared by : Prof. DR. Ishak Aris and Syed Khairil Syed Kharuddin

Modified by: Hadrihl